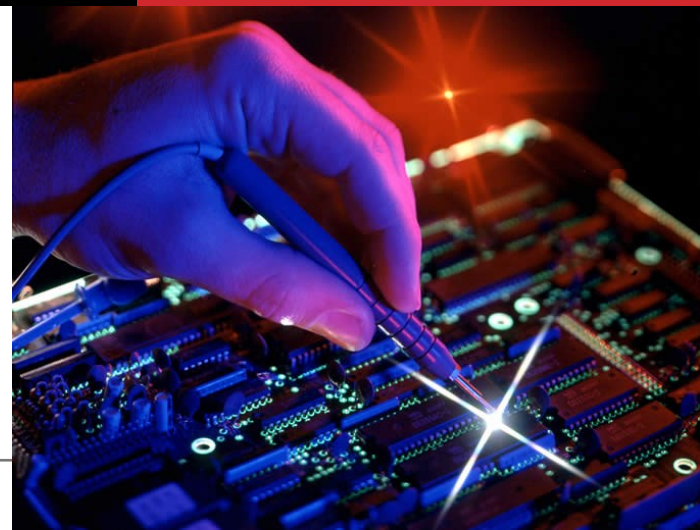




# Advanced Computer Architecture

## FSM DESIGN EXERCISE

Dennis A. N. Gookyi





# CONTENTS

## ❖ FSM Design Exercise

- Candy Vending Machine






# FSM DESIGN EXAMPLE
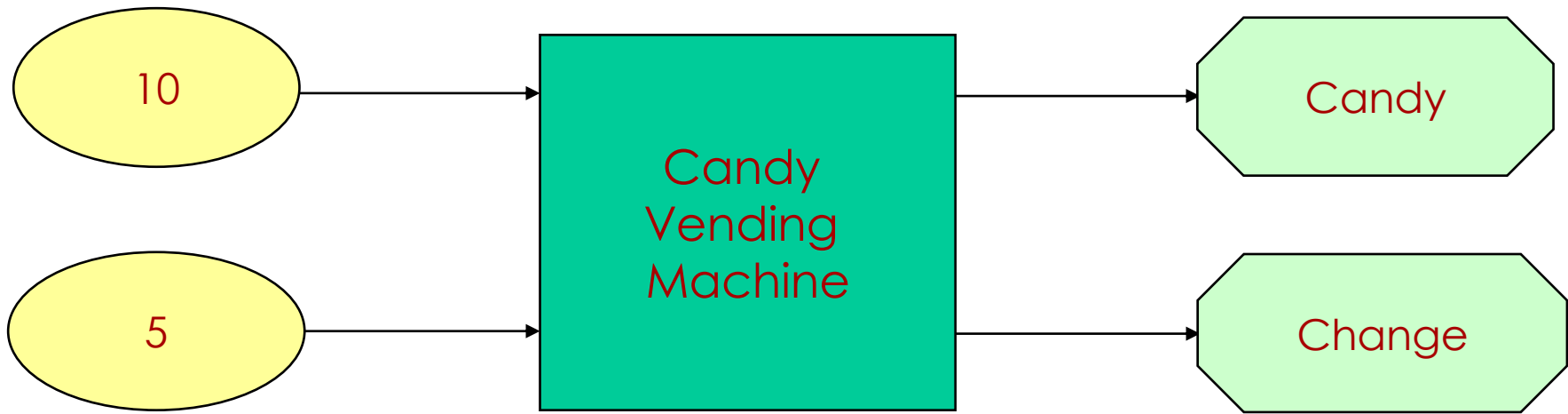
## ❖ Design Specification: Candy Vending Machine

- ❑ One candy cost 20
- ❑ Only 10 and 5 coins are accepted
- ❑ When money exceeding 20 comes in, candy and change are released
  - The money received cannot exceed 25 won





# FSM DESIGN EXAMPLE


## ❖ Input/Output Specifications

### □ Inputs

- T (Ten): Enter 10 coin
- F (Five): Enter 5 coin
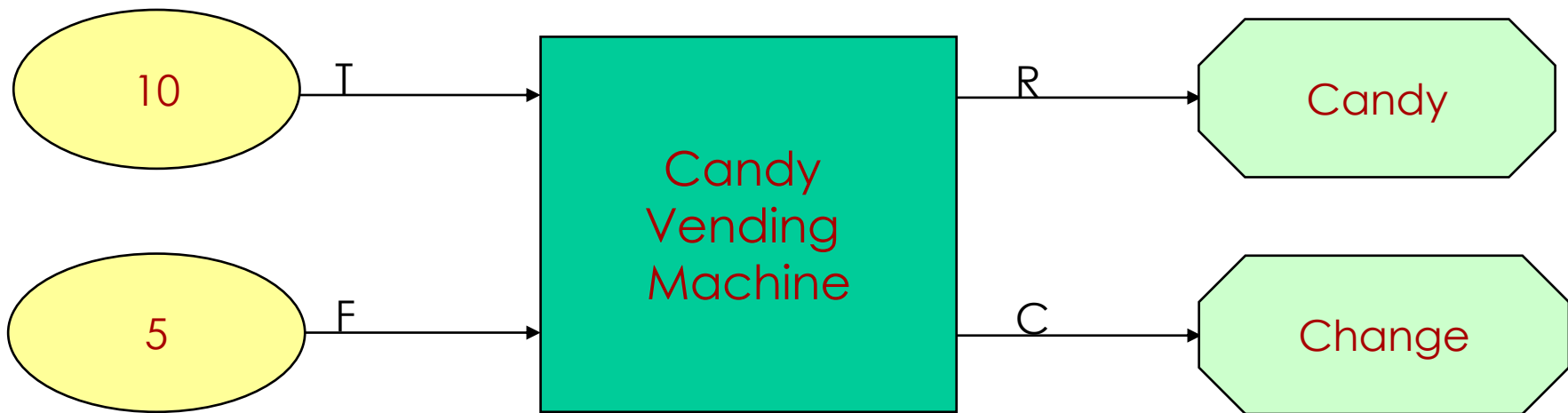
### □ Outputs

- R (Release): Candy release
- C (Change): Change release





# FSM DESIGN EXAMPLE

- ❖ Design the FSM state diagram for the Candy Vending Machine using either Mealy or Moore-type FSM
- ❖ Design the FSM state transition table
  - Encode the state transition table using binary encoding
  - Derive Boolean equations from the state transition table
- ❖ Design the FSM output table
  - Encode the output table using binary encoding
  - Derive Boolean equations from the output table
- ❖ Draw the FSM schematic arranged as the architecture below:

