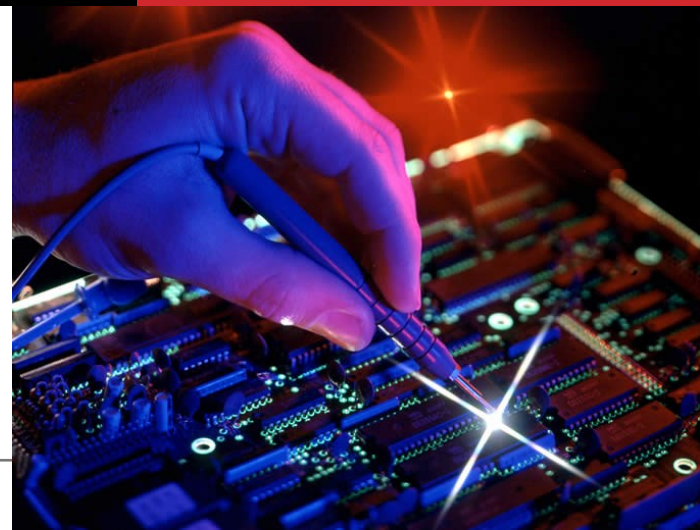




# Advanced Computer Architecture

## SEQUENTIAL LOGIC DESIGN

Dennis A. N. Gookyi





# CONTENTS


## ❖ Sequential Logic Design





# BIG PICTURE: BUILDING A PROCESSOR


## ❖ Single cycle processor

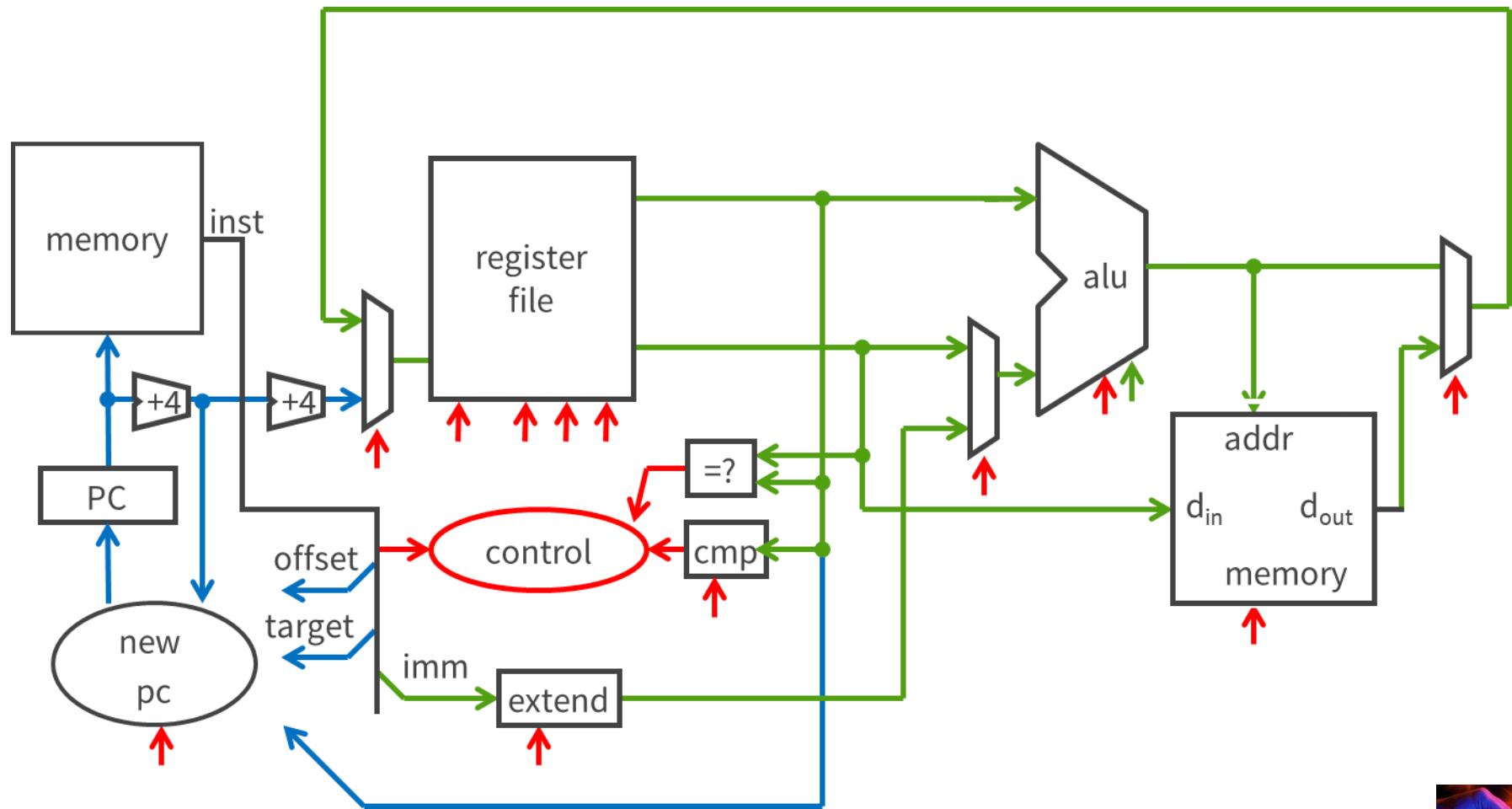


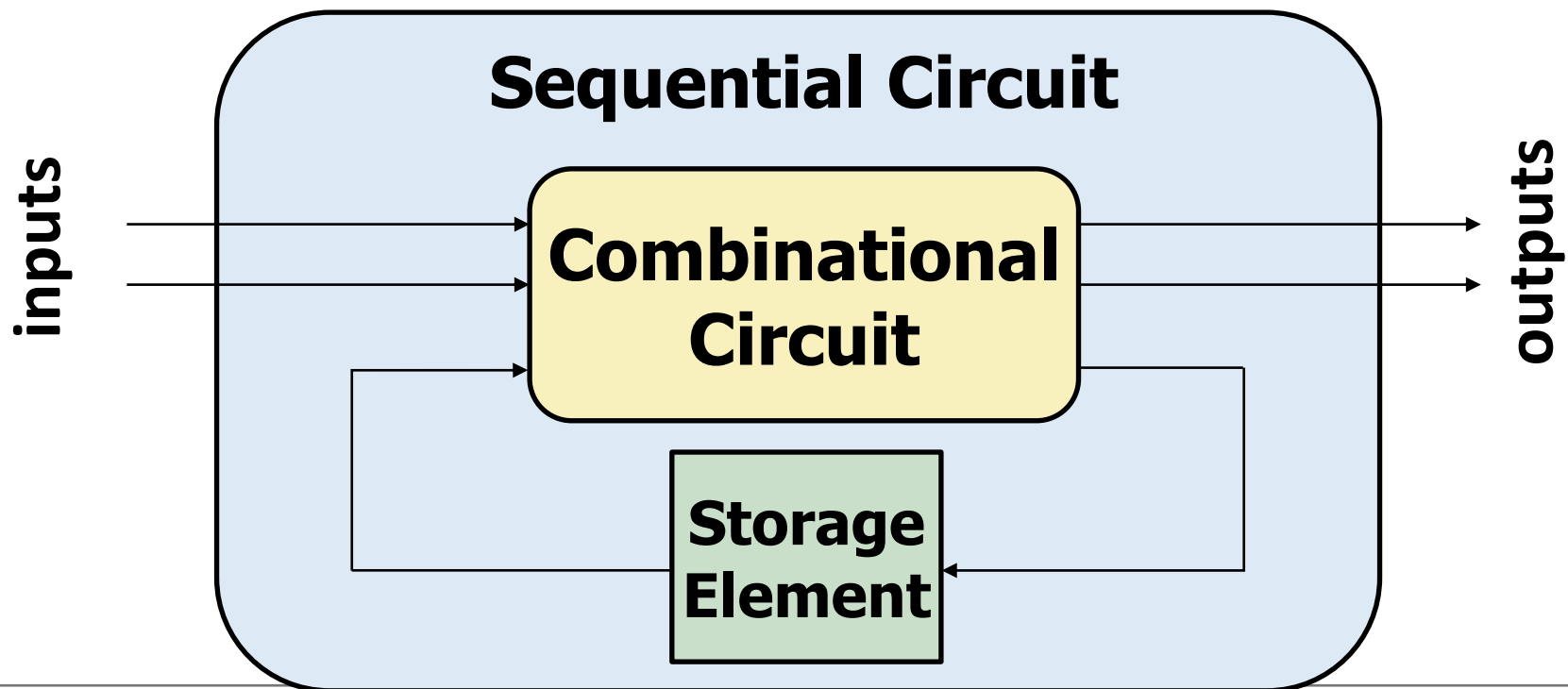
# INTRODUCTION

- ❖ Combinational circuit output depends **only** on **current** input
- ❖ We want circuits that produce output depending on **current** and **past** input values – circuits with **memory**
- ❖ How can we design a circuit that **stores information**?





# SEQUENTIAL LOGIC CIRCUITS

- ❖ We have examined designs of circuit elements that can store information
- ❖ Now, we will use these elements to build circuits that remember past inputs



## Combinational

Only depends on current inputs



## Sequential

Opens depending on past inputs





# STATE


- ❖ In order for this lock to work, it has to keep track (**remember**) of the past events!
- ❖ If passcode is R13-L22-R3, sequence of **states** to unlock:
  - A. The lock is not open (locked), and no relevant operations have been performed
  - B. Locked but user has completed R13
  - C. Locked but user has completed R13-L22
  - D. Unlocked: user has completed R13-L22-R3
- ❖ The **state** of a system is a snapshot of all relevant elements of the system at the moment of the snapshot
  - To open the lock, **states A-D must be completed in order**
  - If anything else happens (e.g., L5), lock **returns** to state A




 
# STATE DIAGRAM

- ❖ Completely describes the operation of the sequential lock



Passcode: **R13-L22-R3**

- ❖ We will understand “state diagrams” fully later today







# STATE DIAGRAM

## ❖ Asynchronous vs. Synchronous State Changes

- Sequential lock we saw is an asynchronous “machine”
  - State transitions occur when they occur
  - There is nothing that synchronizes when each state transition must occur
- Most modern computers are synchronous “machines”
  - State transitions take place after fixed units of time
  - Controlled in part by a clock, as we will see soon
- These are two different design paradigms, with tradeoffs









# STATE DIAGRAM

❖ A standard Swiss traffic light has 4 states

 - A. Green
- B. Yellow
- C. Red
- D. Red and Yellow




 ❖ The sequence of these states are always as follows





# STATE DIAGRAM - CLOCK

 

- ❖ When should the light change from one state to another?
- ❖ We need a **clock** to dictate when to change state
  - Clock signal alternates between 0 & 1


 


Figure 3.28 A clock signal.

 



# STATE DIAGRAM - CLOCK



- ❖ When should the light change from one state to another?
- ❖ We need a **clock** to dictate when to change state

- ☐ Clock signal alternates between 0 & 1



- ❖ At the start of a clock cycle (), system state changes
  - ☐ During a clock cycle, the state stays constant
  - ☐ In this traffic light example, we are assuming the traffic light stays in each state an equal amount of time





# STATE DIAGRAM - CLOCK

- ❖ Clock is a general mechanism that triggers transition from one state to another in a (synchronous) sequential circuit
- ❖ Clock synchronizes state changes across many sequential circuit elements
- ❖ Combinational logic evaluates for the length of the clock cycle
- ❖ Clock cycle should be chosen to accommodate maximum combinational circuit delay





# STATE DIAGRAM

## ❖ Asynchronous vs. Synchronous State Changes

- Sequential lock we saw is an asynchronous “machine”
  - State transitions occur when they occur
  - There is nothing that synchronizes when each state transition must occur
  
- Most modern computers are synchronous “machines”
  - State transitions take place after fixed units of time
  - Controlled in part by a clock, as we will see soon
  
- These are two different design paradigms, with tradeoffs
  - Synchronous control can be easier to get correct when the system consists of many components and many states
  - Asynchronous control can be more efficient (no clock overheads)





# FINITE STATE MACHINE (FSM)

- ❖ What is a Finite State Machine (FSM)?
  - A discrete-time model of a stateful system
  - Each state represents a snapshot of the system at a given time
- ❖ An FSM pictorially shows
  - The set of all possible states that a system can be in
  - How the system transitions from one state to another
- ❖ An FSM can model
  - A traffic light, an elevator, fan speed, a microprocessor, etc.
- ❖ An FSM enables us to pictorially think of a stateful system using simple diagrams





# FINITE STATE MACHINE (FSM)

❖ FSM consist of five elements:

- A finite number of states
  - State: snapshot of all relevant elements of the system at the time of the snapshot
- A finite number of external inputs
- A finite number of external outputs
- An explicit specification of all state transitions
  - How to get from one state to another
- An explicit specification of what determines each external output value







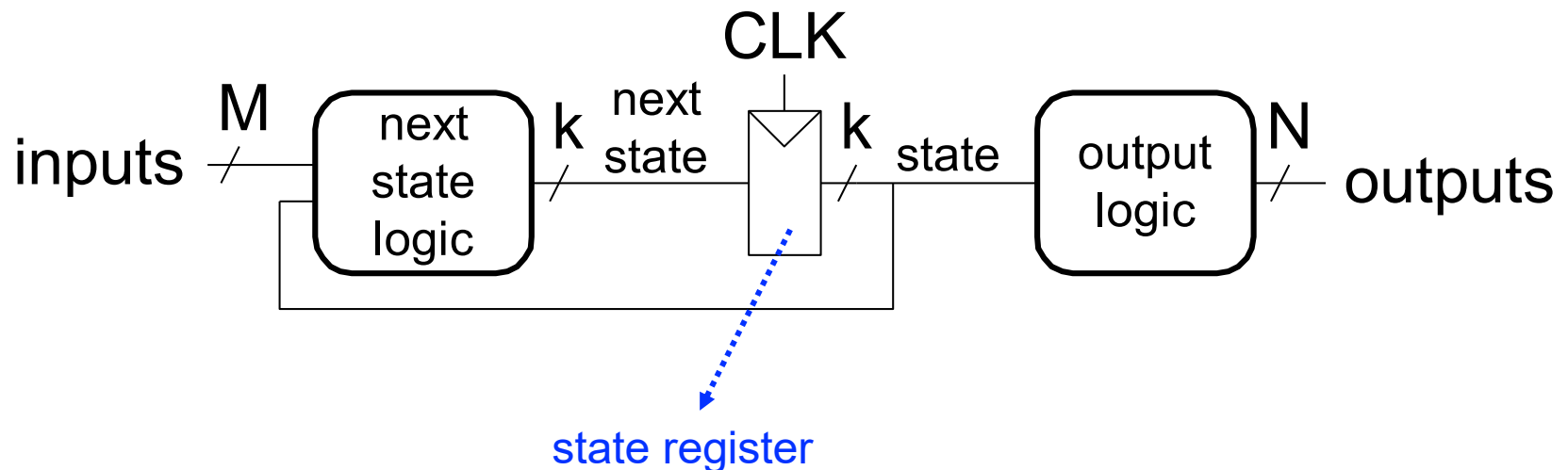
# FINITE STATE MACHINE (FSM)

❖ Each FSM consists of three separate parts:

- next state logic
- state register
- output logic



At the beginning of the clock cycle, next state is latched into the state register






# FINITE STATE MACHINE (FSM)


 
## ❖ Sequential Circuits

- State register(s)
  - Store the current state and
  - Load the next state at the clock edge


  
## ❖ Combinational Circuits

- Next state logic
  - Determines what the next state will be
- Output logic
  - Generates the outputs







# FINITE STATE MACHINE (FSM)

- ❖ Next state is determined by the current state and the inputs
- ❖ Two types of finite state machines differ in the output logic:
  - Moore FSM: outputs depend only on the current state
  - Mealy FSM: outputs depend on the current state and the inputs

## Moore FSM

 

## Mealy FSM

 



# FINITE STATE MACHINE (FSM)

## ❖ Example: “Smart” traffic light controller

### □ 2 inputs:


- Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there's traffic)

### □ 2 outputs:

- Lights:  $L_A$ ,  $L_B$  (Red, Yellow, Green)
 
### □ State can change every 5 seconds

- Except if green and traffic, stay green






# FINITE STATE MACHINE (FSM)

❖ Inputs: CLK, Reset,  $T_A$ ,  $T_B$

❖ Outputs:  $L_A$ ,  $L_B$


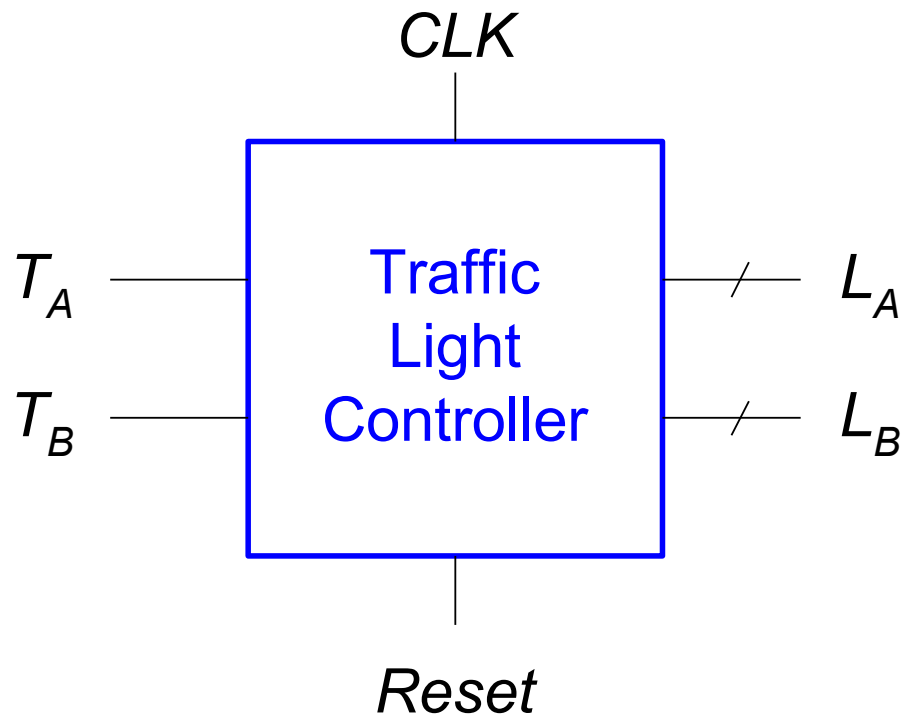




# FINITE STATE MACHINE (FSM)

❖ Moore FSM: outputs labeled in each state

- States: Circles
- Transitions: Arcs

 
 




# FINITE STATE MACHINE (FSM)

❖ Moore FSM: outputs labeled in each state

- States: Circles
- Transitions: Arcs

  







# FINITE STATE MACHINE (FSM)

❖ Moore FSM: outputs labeled in each state

- States: Circles
- Transitions: Arcs

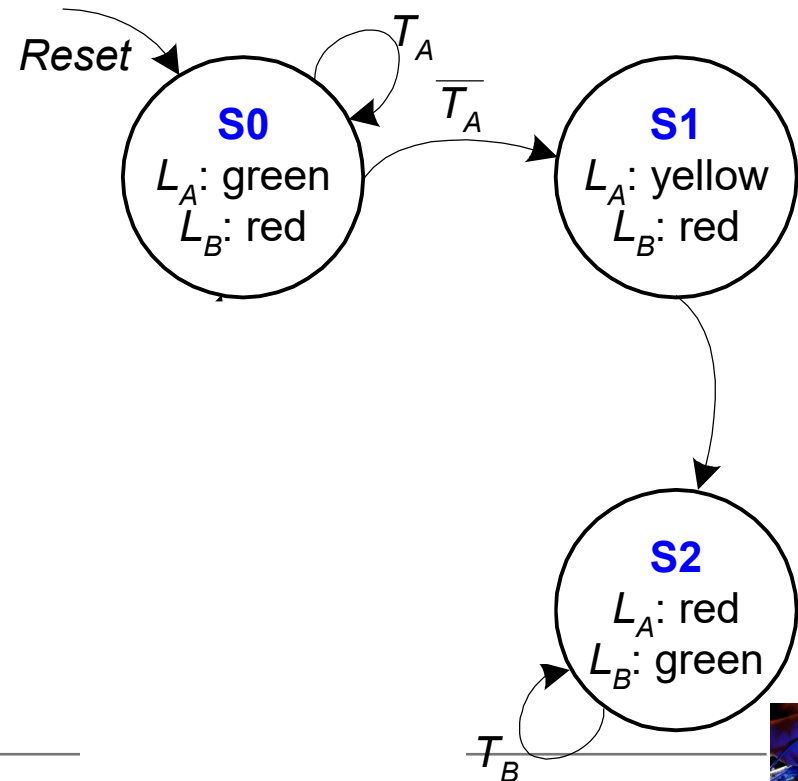
 




# FINITE STATE MACHINE (FSM)

❖ Moore FSM: outputs labeled in each state

- States: Circles
- Transitions: Arcs

 
 




# FINITE STATE MACHINE (FSM)

❖ Moore FSM: outputs labeled in each state


- States: Circles
- Transitions: Arcs

 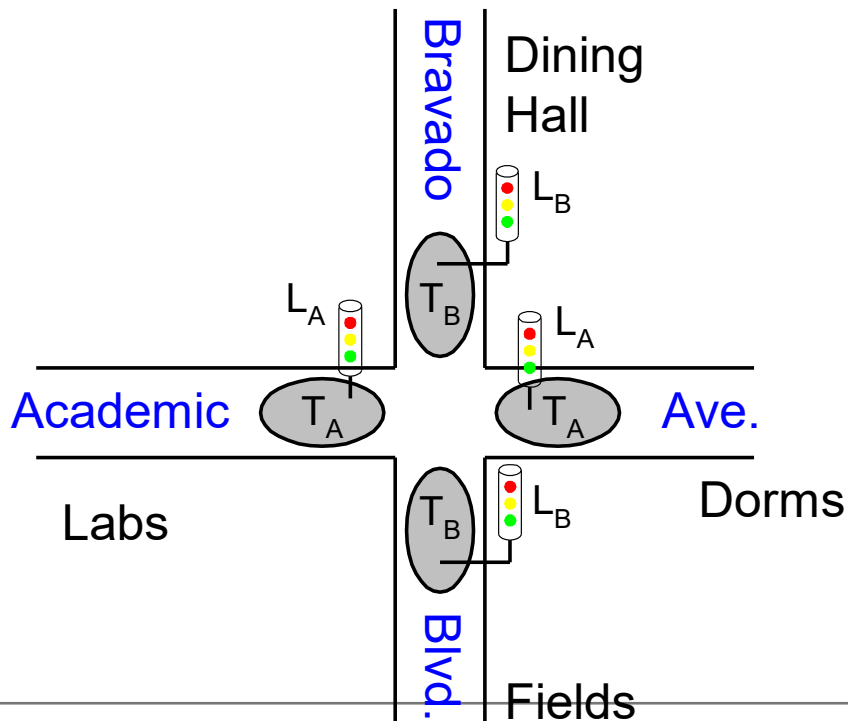




# FSM – STATE TRANSITION TABLE

## ❖ State transition table

 


Current State	Inputs		Next State
S	$T_A$	$T_B$	$S'$
S0	0	X	
S0	1	X	
S1	X	X	
S2	X	0	
S2	X	1	
S3	X	X	

 


# FSM – STATE TRANSITION TABLE

## ❖ State transition table

 


Current State	Inputs		Next State
S	$T_A$	$T_B$	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

 




# FSM – STATE TRANSITION TABLE

## ❖ State transition table

 


Current State	Inputs		Next State
S	$T_A$	$T_B$	S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

State	Encoding
S0	00
S1	01
S2	10
S3	11

 


# FSM – STATE TRANSITION TABLE

## ❖ State transition table

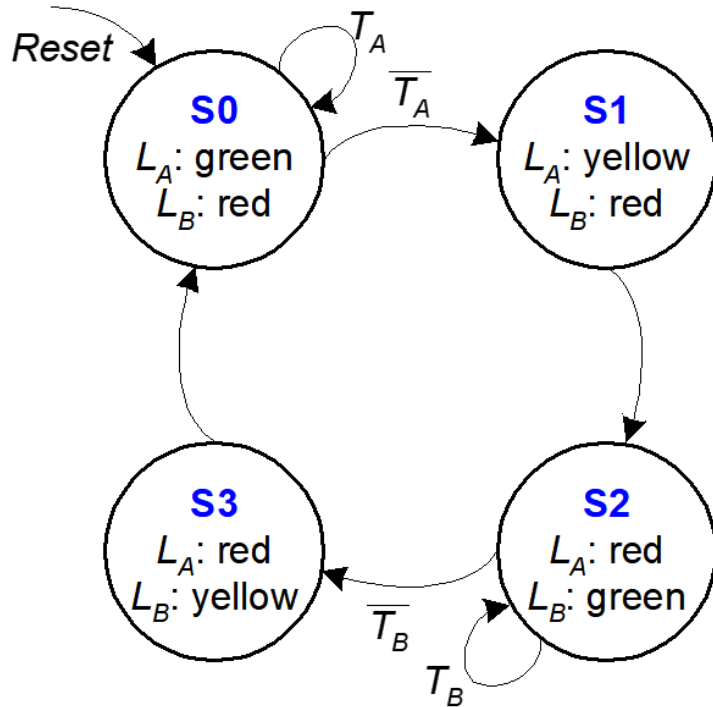

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0


State	Encoding
S0	00
S1	01
S2	10
S3	11

 



# FSM – STATE TRANSITION TABLE

## ❖ State transition table

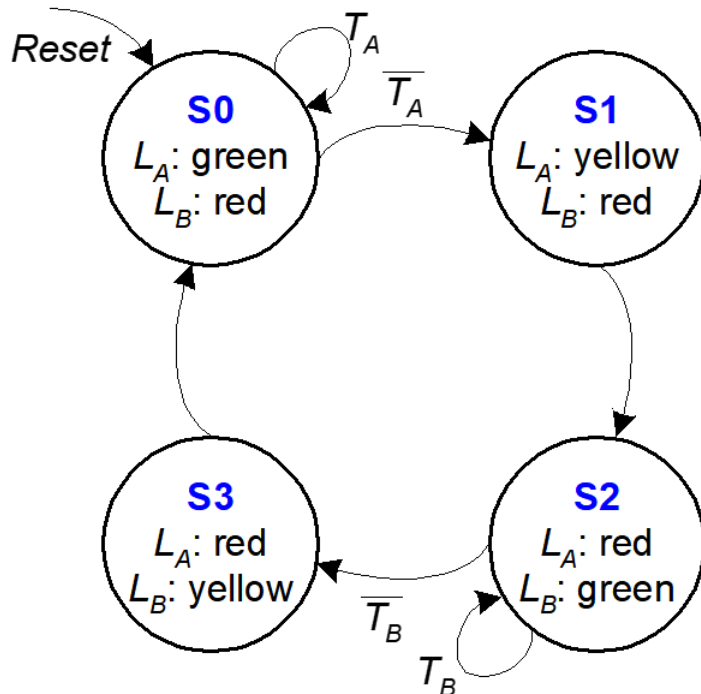

$S'_1 = ?$


Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11



# FSM – STATE TRANSITION TABLE

## ❖ State transition table

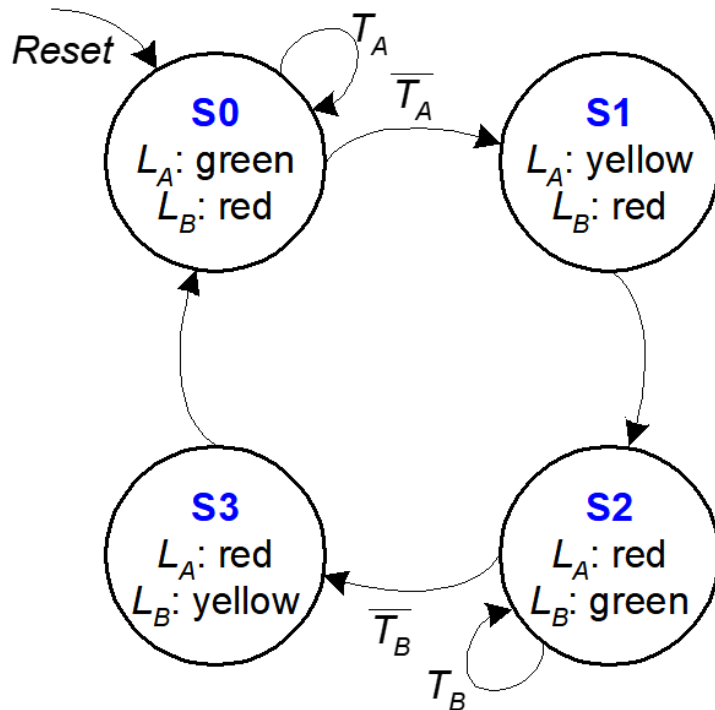

Current State		Inputs		Next State	
S <sub>1</sub>	S <sub>0</sub>	T <sub>A</sub>	T <sub>B</sub>	S' <sub>1</sub>	S' <sub>0</sub>
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0


State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\bar{S}_1 \cdot S_0) + (S_1 \cdot \bar{S}_0 \cdot \bar{T}_B) + (S_1 \cdot \bar{S}_0 \cdot T_B)$$



# FSM – STATE TRANSITION TABLE

## ❖ State transition table

 

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

$$S'_1 = (\overline{S_1} \cdot S_0) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B}) + (S_1 \cdot \overline{S_0} \cdot T_B)$$


$$S'_0 = ?$$





# FSM – STATE TRANSITION TABLE

## ❖ State transition table

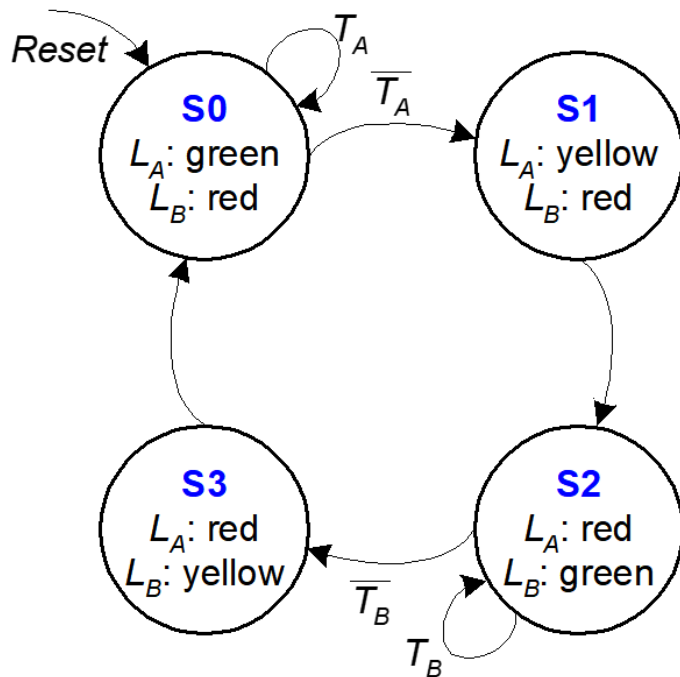

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11


$$S'_1 = (\bar{S}_1 \cdot S_0) + (S_1 \cdot \bar{S}_0 \cdot \bar{T}_B) + (S_1 \cdot \bar{S}_0 \cdot T_B)$$

$$S'_0 = (\bar{S}_1 \cdot \bar{S}_0 \cdot \bar{T}_A) + (S_1 \cdot \bar{S}_0 \cdot \bar{T}_B)$$



# FSM – STATE TRANSITION TABLE

## ❖ State transition table

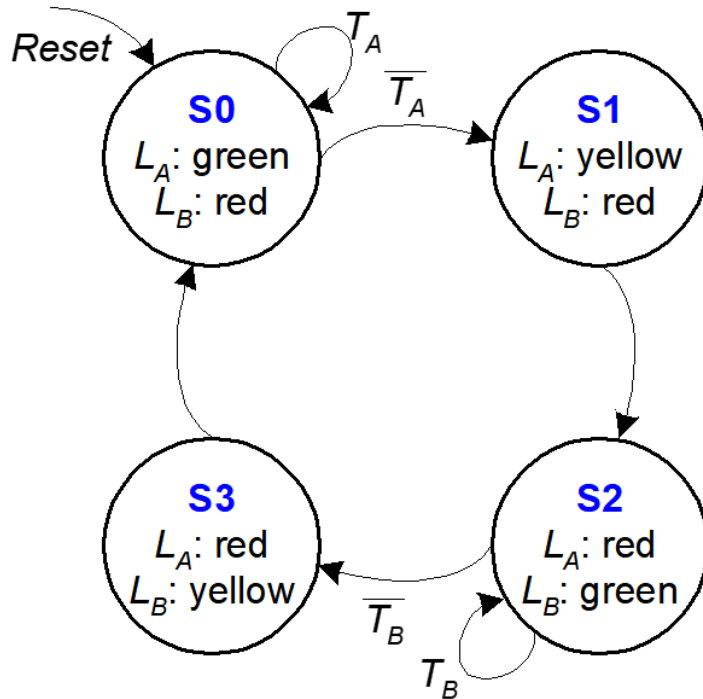

Current State		Inputs		Next State	
$S_1$	$S_0$	$T_A$	$T_B$	$S'_1$	$S'_0$
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11


$$S'_1 = S_1 \text{ xor } S_0 \quad \text{(Simplified)}$$

$$S'_0 = (\bar{S}_1 \cdot \bar{S}_0 \cdot \bar{T}_A) + (S_1 \cdot \bar{S}_0 \cdot \bar{T}_B)$$




# FSM – OUTPUT TABLE

## ❖ Output table

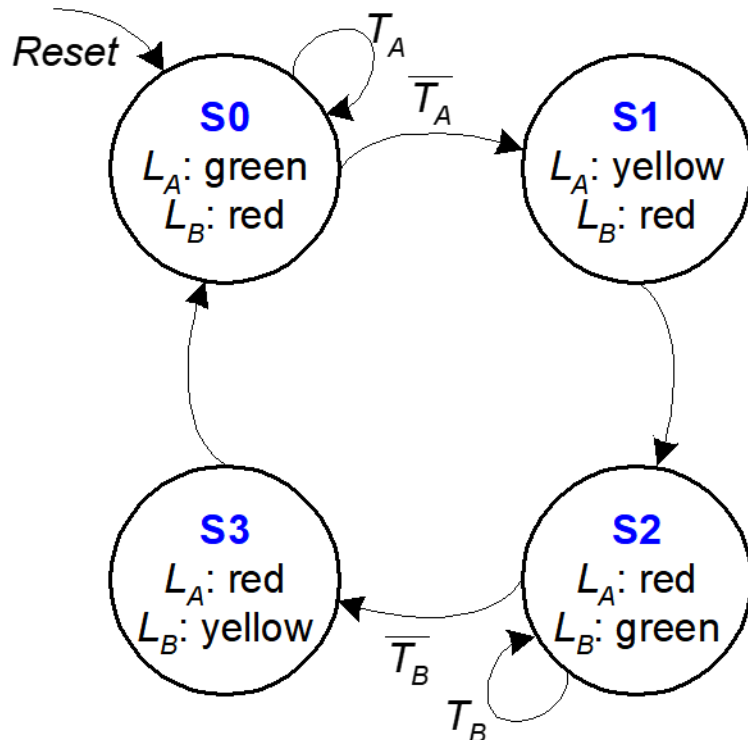


Current State		Outputs	
$S_1$	$S_0$	$L_A$	$L_B$
0	0	green	red
0	1	yellow	red
1	0	red	green
1	1	red	yellow

 


# FSM – OUTPUT TABLE

## ❖ Output table

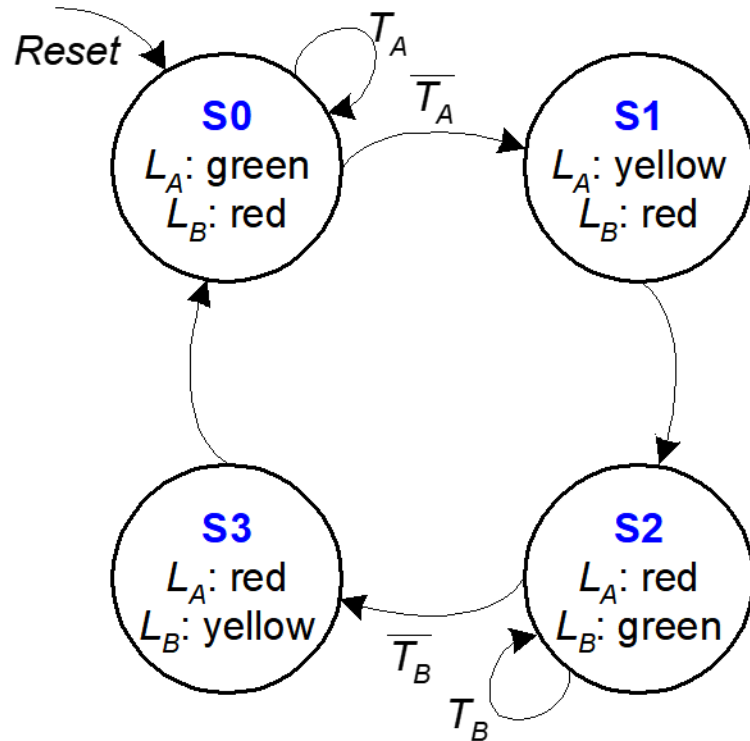

Current State		Outputs	
$S_1$	$S_0$	$L_A$	$L_B$
0	0	green	red
0	1	yellow	red
1	0	red	green
1	1	red	yellow

 


Output	Encoding
green	00
yellow	01
red	10



# FSM – OUTPUT TABLE

## ❖ Output table

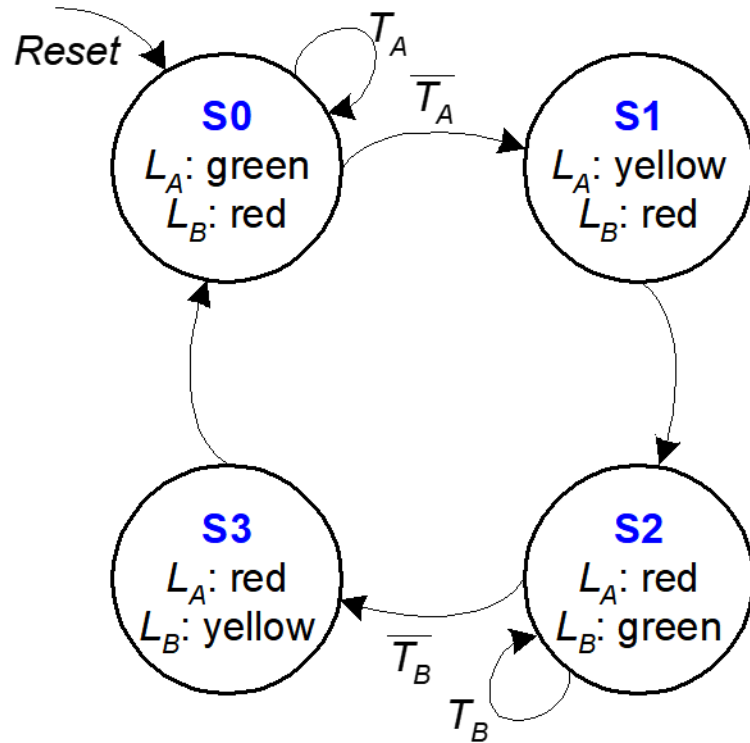


Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

# FSM – OUTPUT TABLE

## ❖ Output table

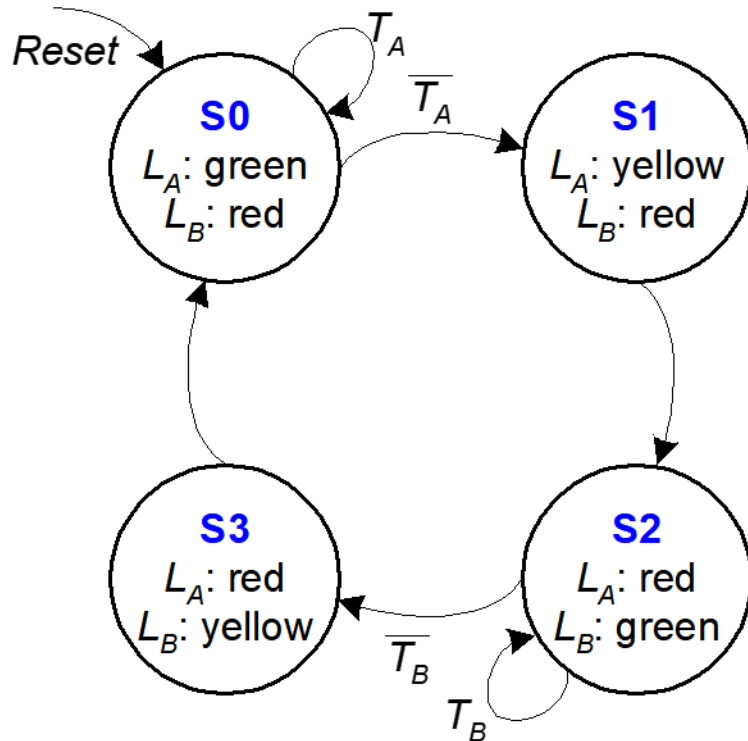

$$L_{A1} = S_1$$


$$L_{A0} = \overline{S_1} \cdot S_0$$

Current State		Outputs			
S <sub>1</sub>	S <sub>0</sub>	L <sub>A1</sub>	L <sub>A0</sub>	L <sub>B1</sub>	L <sub>B0</sub>
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

# FSM – OUTPUT TABLE

## ❖ Output table

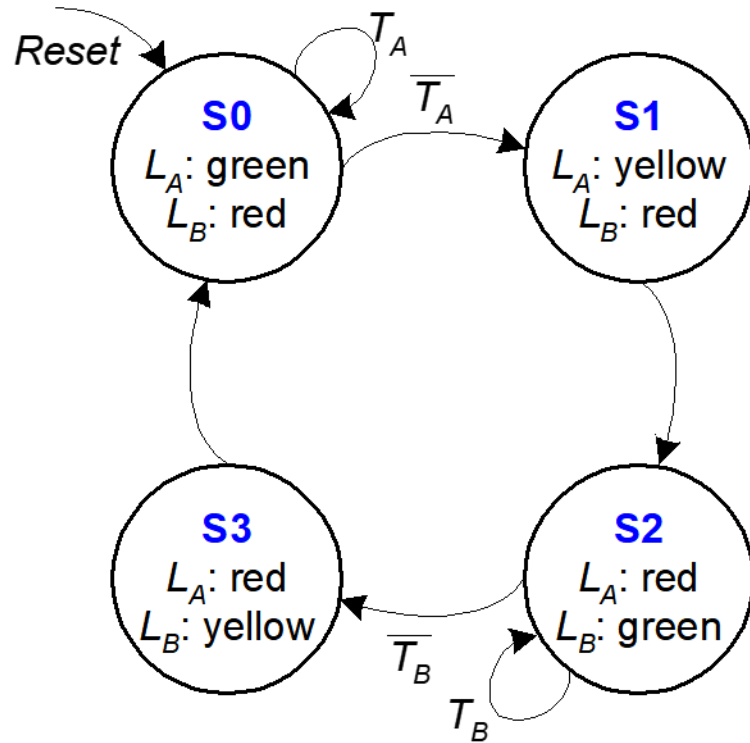

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1


$$\begin{aligned}
 L_{A1} &= S_1 \\
 L_{A0} &= \overline{S_1} \cdot S_0 \\
 L_{B1} &= \overline{S_1}
 \end{aligned}$$

Output	Encoding
green	00
yellow	01
red	10



# FSM – OUTPUT TABLE

## ❖ Output table

 

Current State		Outputs			
$S_1$	$S_0$	$L_{A1}$	$L_{A0}$	$L_{B1}$	$L_{B0}$
0	0	0	0	1	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	0	0	1

Output	Encoding
green	00
yellow	01
red	10

$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1} \cdot S_0$$

$$L_{B1} = \overline{S_1}$$


$$L_{B0} = S_1 \cdot S_0$$





# FSM – SCHEMATIC


## ❖ Overview

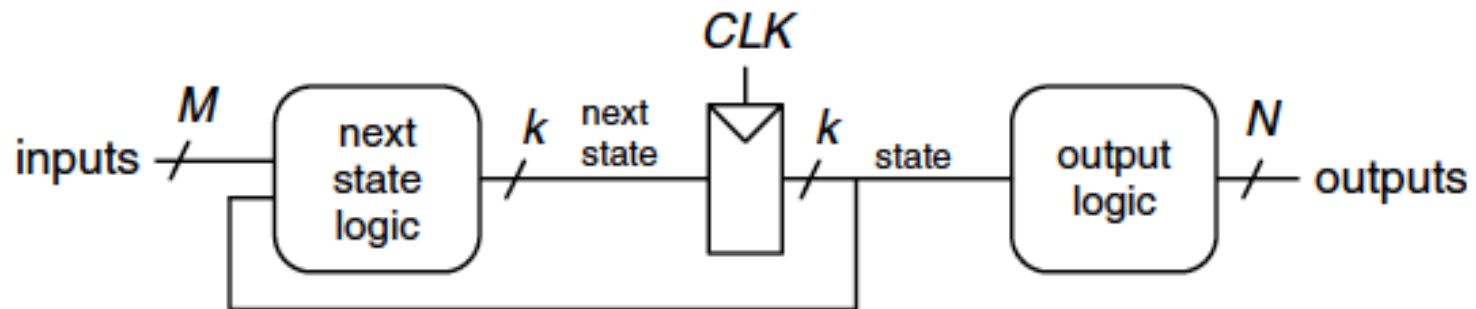



# FSM – SCHEMATIC


## ❖ State register

 



# FSM – SCHEMATIC

## ❖ Next state logic

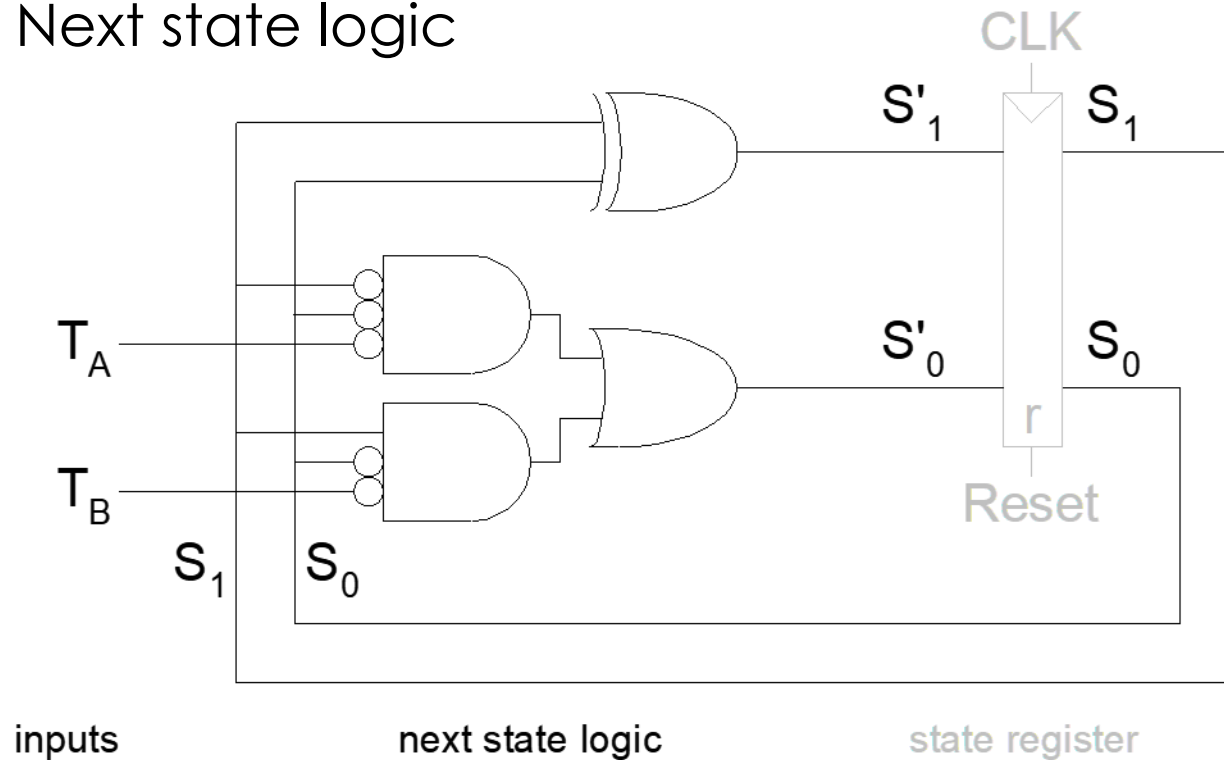

$$S'_1 = S_1 \text{ xor } S_0$$


$$S'_0 = (\overline{S_1} \cdot \overline{S_0} \cdot \overline{T_A}) + (S_1 \cdot \overline{S_0} \cdot \overline{T_B})$$





# FSM – SCHEMATIC

## ❖ Output logic

 

$$\begin{aligned} L_{A1} &= S_1 \\ L_{A0} &= \overline{S_1} \cdot S_0 \\ L_{B1} &= \overline{S_1} \\ L_{B0} &= S_1 \cdot S_0 \end{aligned}$$








# FSM – TIMING DIAGRAM

## ❖ Timing diagram

 



CLK\_ \_  
Reset\_ \_  
T<sub>A</sub> \_  
T<sub>B</sub> \_  
S' \_  
1:0 \_  
S \_  
1:0 \_  
L<sub>A</sub> 1:0 \_  
L<sub>B</sub> 1:0 \_





# FSM – TIMING DIAGRAM



## ❖ Timing diagram

  



# FSM – TIMING DIAGRAM



## ❖ Timing diagram

  



# FSM – TIMING DIAGRAM



## ❖ Timing diagram

  



# FSM – TIMING DIAGRAM



## ❖ Timing diagram

  



# FSM – TIMING DIAGRAM



## ❖ Timing diagram

  



# FSM – TIMING DIAGRAM



## ❖ Timing diagram

  



# FSM – TIMING DIAGRAM

## ❖ Timing diagram

 
 






# FSM – TIMING DIAGRAM



## ❖ Timing diagram

  



# FSM – TIMING DIAGRAM


## ❖ Timing diagram

  


 
# FSM – STATE ENCODING

- ❖ How do we encode the state bits?
- ❖ Three common state binary encodings with different tradeoffs
  - ☐ Fully Encoded
  - ☐ 1-Hot Encoded
  - ☐ Output Encoded
- ❖ Let's see an example Swiss traffic light with 4 states
  - ☐ Green, Yellow, Red, Yellow+Red





# FSM – STATE ENCODING

## ❖ Binary Encoding (Full Encoding):

- Use the minimum possible number of bits
  - Use  $\log_2(\text{num\_states})$  bits to represent the states
- Example state encodings: 00, 01, 10, 11
- Minimizes # flip-flops, but not necessarily output logic or next state logic





# FSM – STATE ENCODING

## ❖ One-Hot Encoding:

- Each bit encodes a different state
  - Uses num\_states bits to represent the states
  - Exactly 1 bit is “hot” for a given state
- Example state encodings: 0001, 0010, 0100, 1000
- Simplest design process – very automatable
- Maximizes # flip-flops, minimizes next state logic





# FSM – STATE ENCODING

## ❖ Output Encoding:

- Outputs are directly accessible in the state encoding
- For example, since we have 3 outputs (light color), encode state with 3 bits, where each bit represents a color
- Example states: 001, 010, 100, 110
  - Bit0 encodes green light output,
  - Bit1 encodes yellow light output
  - Bit2 encodes red light output
- Minimizes output logic
- Only works for Moore Machines (output function of state)






# FSM – STATE ENCODING

- ❖ The designer must carefully choose an encoding scheme to optimize the design under given constraints





## ❖ sdsd

 

### State Transition Table

Current State	Inputs		Next State
	$T_A$	$T_B$	
S			S'
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

State	Encoding
S0	0001
S1	0010
S2	0100
S3	1000

### Output Table

Current State	LA
S0	green
S1	yellow
S2	red
S3	red

Output	Encoding
green	0001
yellow	0010
red	0100

